

Complex Impedance

①

Complex # $i = j = \sqrt{-1}$

Seems strange at first, but simple consequence of algebra


Integers (Counting) $\Rightarrow$ Addition, ~~subtraction~~ multiplication, Powers.

Leads to inverse operations $\Rightarrow$ subtraction, division, Square root
 $\downarrow$ $\downarrow$
Negative #'s Irrational #'s

this set of operations cannot solve ~~every~~ every algebraic eqn.

Complex # $\Rightarrow x^2 = -1$
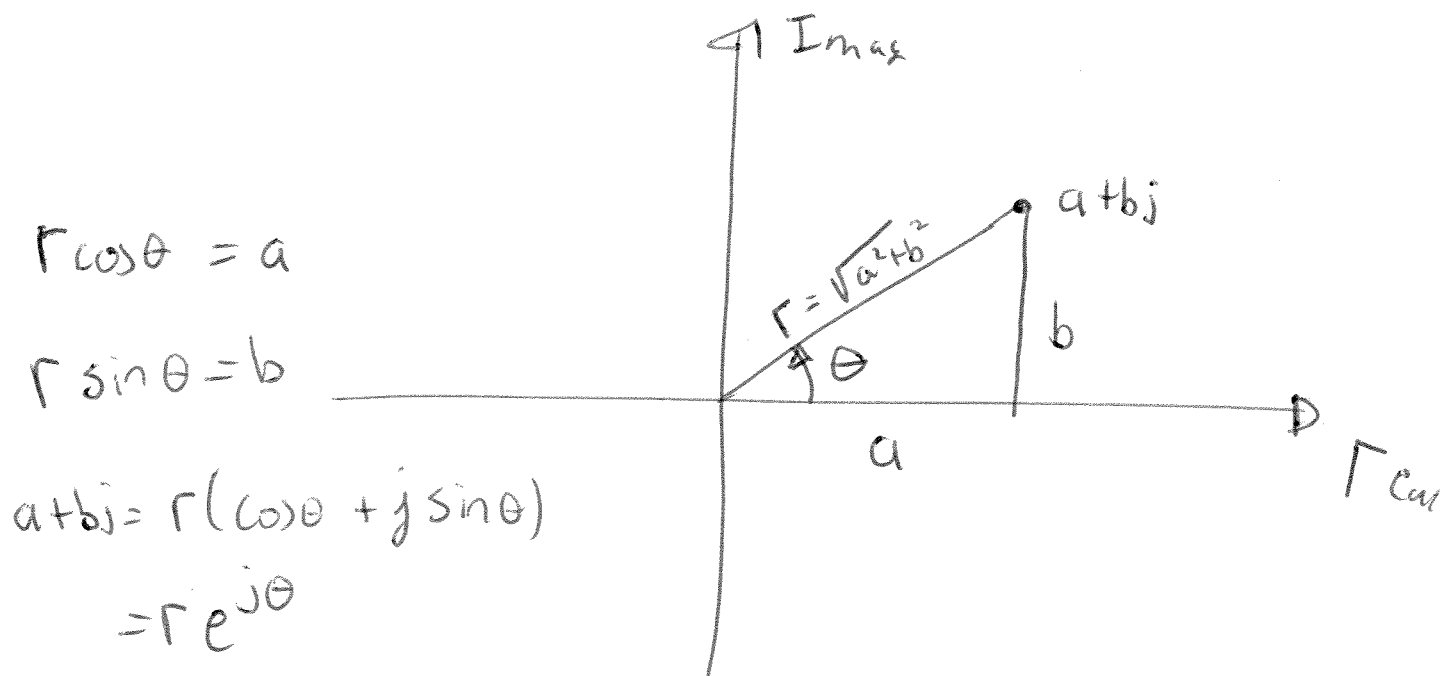
$$e^{j\theta} = \cos \theta + j \sin \theta \quad (\text{Proved in linearity})$$




(2)

Since $e^{j\theta} = \cos\theta + j\sin\theta$


We'll use $e^{j\omega t}$ to represent sinusoids.
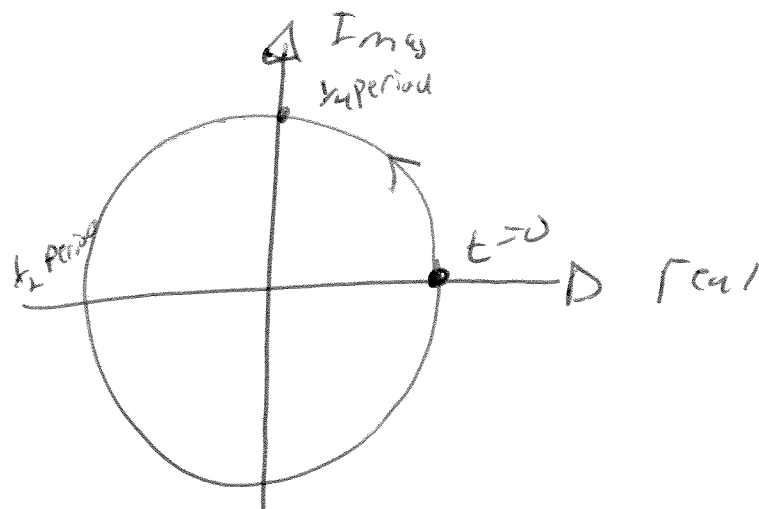
$$V(t) = e^{j\omega t} = \cos\omega t + j\sin\omega t$$



if we add a # out front, a complex amplitude

$$V(t) = \vec{V} e^{j\omega t}$$

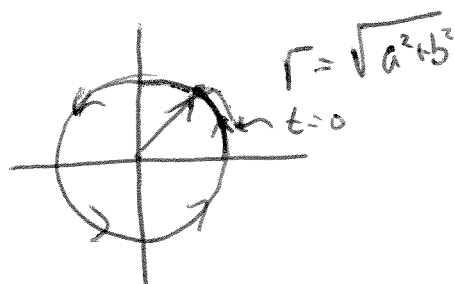

Linear Eqns $\Rightarrow$ if we assume complex Solns

then real + imag parts are separable, both must be satisfied.

(3)

Can ~~we~~ take real part at the end.

$$V(t) = \bar{V} e^{j\omega t} \Rightarrow V(t) = \text{Real}(\bar{V} e^{j\omega t})$$

$$\bar{V} = (a + bj)$$

$$V(t) = \text{Real} \left[(a + bj) (\cos \omega t + j \sin \omega t) \right]$$

$$= \text{Real} \left[(a \cos \omega t - b \sin \omega t) + j (b \cos \omega t + a \sin \omega t) \right]$$


$$V(t) = a \cos \omega t - b \sin \omega t$$

$$V(t) = \sqrt{a^2 + b^2} \left[\cos(\omega t) \frac{a}{\sqrt{a^2 + b^2}} - \frac{b}{\sqrt{a^2 + b^2}} \sin \omega t \right]$$

trig identity

$$\cos(\omega t + \phi) = \cos \omega t \cos \phi - \sin \omega t \sin \phi$$

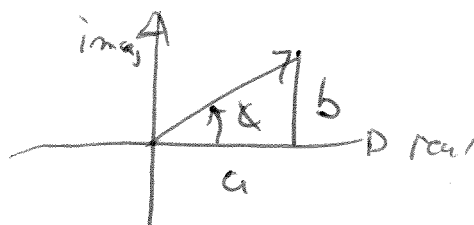
$$\frac{a}{\sqrt{a^2 + b^2}} = \cos \phi \quad \frac{b}{\sqrt{a^2 + b^2}} = \sin \phi$$



Phase is somehow
built into
complex amplitude

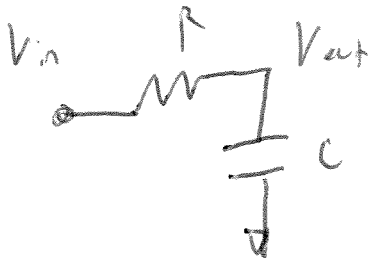(4)

Solve some problems and then come back to basics.



Sinuso. Steady state response

$$V_{in}(t) = \tilde{V}_{in} e^{j\omega t}$$

$$V_{out}(t) = \tilde{V}_{out} e^{j\omega t}$$

$$\tilde{I} = \frac{V_{in} - V_{out}}{R} = C \frac{dV_o}{dt}$$

$$RC \frac{dV_o}{dt} = V_{in}(t) - V_{out}(t)$$


$$RCj\omega \tilde{V}_o e^{j\omega t} = \tilde{V}_{in} e^{j\omega t} - \tilde{V}_o e^{j\omega t}$$

$$\tilde{V}_{in} = \tilde{V}_o (1 + RCj\omega)$$

$$\boxed{\frac{\tilde{V}_o}{\tilde{V}_{in}} = \frac{1}{1 + RCj\omega}}$$

* complex #

5

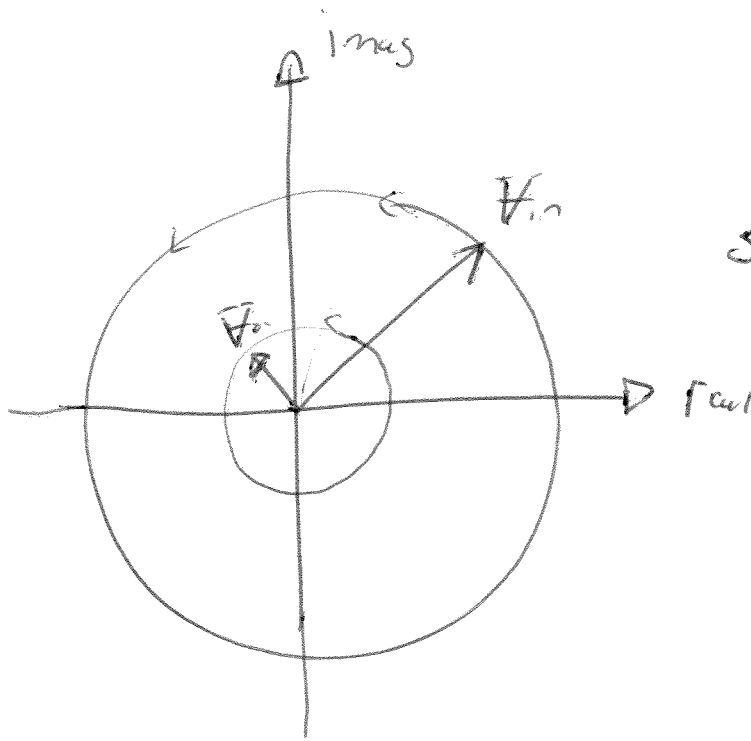

Same freq. around.

Since Starting pt. doesn't matter, only want phase between

$$\text{Set } V_{in} = 1$$


then phase is $\arctan\left(\frac{b}{a}\right)$

$$\text{amp. is } \sqrt{a^2 + b^2}$$

Demo plot in matlab!

(6)

A simpler way
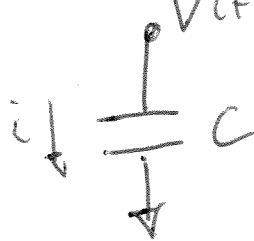
$$V(t) = \bar{V} e^{j\omega t}$$


$$i(t) = I e^{j\omega t}$$

$$i(t) = C \frac{dV(t)}{dt}$$


$$I = j\omega C \bar{V}$$

$$\bar{V} = I Z \quad \text{where} \quad \boxed{Z = \frac{1}{j\omega C}}$$

↑
Impedance.

for resistor $\boxed{Z = R}$

Networks of R, C use impedance, and same rules for series and parallel apply!

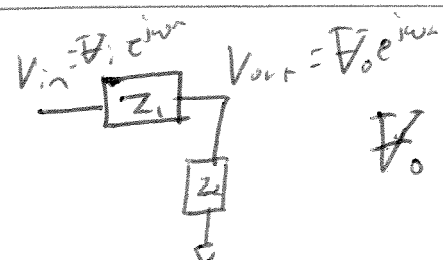
ex  $\equiv$ 

$$\bar{V}_0 = \bar{V}_{in} \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{\bar{V}_0}{\bar{V}_{in}} = \frac{1/j\omega C}{1 + j\omega R} = \frac{1}{1 + j\omega RC}$$

$$\text{---} \parallel \text{---} = \frac{\bar{V}_0}{\bar{V}_{in}} = \frac{R}{1/j\omega C + R} = \frac{j\omega RC}{1 + j\omega RC}$$

7

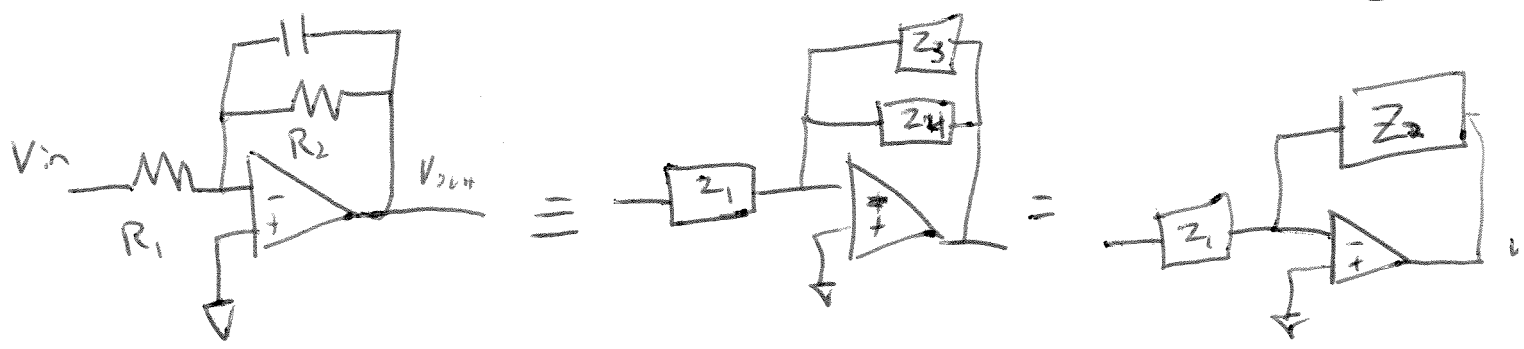

$$\frac{V_{in} - 0}{Z_1} = I = \frac{0 - V_{out}}{Z_2}$$



$$\frac{V_o}{V_{in}} = \frac{Z_2}{Z_1}$$

but $Z_2 = \frac{1}{\frac{1}{Z_3} + \frac{1}{Z_4}} = \frac{1}{\frac{1}{R_2} + j\omega C} = \frac{R_2}{1 + j\omega R_2 C}$

$$\frac{V_o}{V_{in}} = \frac{R_2 / R_1}{1 + j\omega R_2 C}$$

gain + filter.

if time (Do only if time)

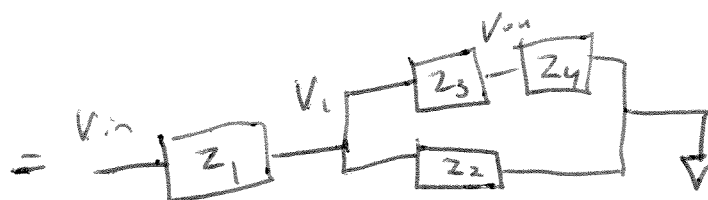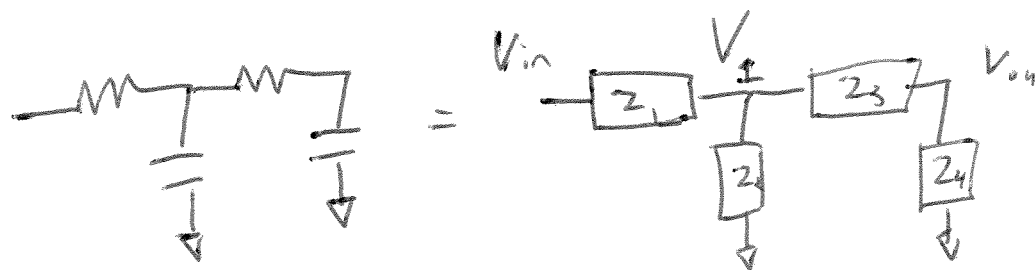

$$V_1 = V_{in} \frac{Z_5}{Z_1 + Z_5}$$


$$Z_5 = \left[\begin{array}{c} Z_3 + Z_4 \\ Z_2 \end{array} \right] = \frac{1}{\frac{1}{Z_2} + \frac{1}{Z_3 + Z_4}} = \frac{Z_2}{1 + \frac{Z_2}{Z_3 + Z_4}}$$

~~V1 = Vin~~

$$V_{out} = V_1 \frac{Z_4}{Z_3 + Z_4} = V_{in} \frac{Z_5}{Z_1 + Z_5} \frac{Z_4}{Z_3 + Z_4}$$

Sallen-Key

9

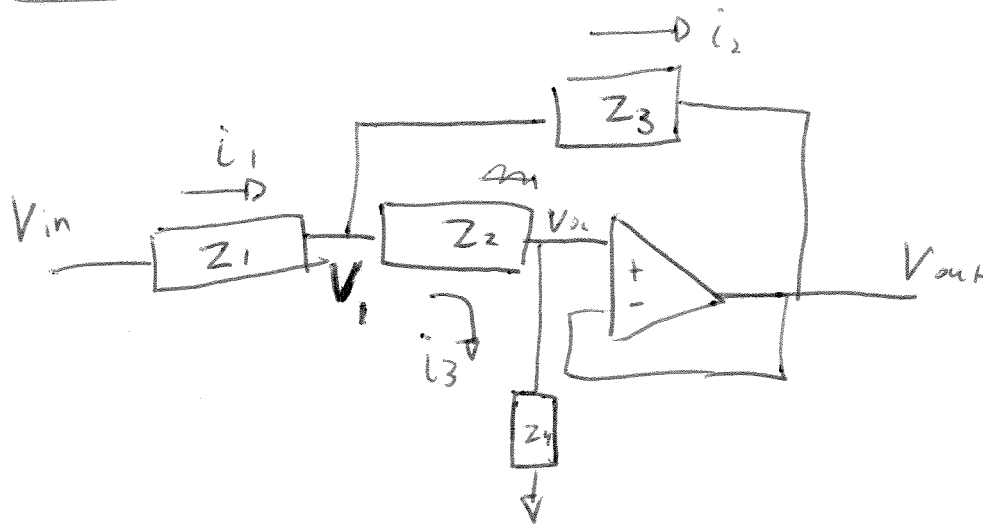

$$i_1 = i_2 + i_3$$

Impedance

$$\frac{V_{in} - V_1}{Z_1} = I_1 = I_2 + I_3$$

$$I_2 = \frac{V_1 - V_{out}}{Z_3}$$

$$I_2 = \frac{Z_2}{Z_3 Z_4} V_{out}$$

$$I_3 = \frac{V_1 - V_{out}}{Z_4} = \frac{V_{out}}{Z_4}$$

$$V_1 - V_{out} = \frac{Z_2}{Z_4} V_{out}$$

$$V_1 = V_{out} \left(1 + \frac{Z_2}{Z_4} \right)$$


(10)

$$\frac{V_{in}}{Z_1} = \frac{V_1}{Z_1} + \frac{Z_2}{Z_3 Z_4} V_{out} + \frac{1}{Z_4} V_{out}$$

$$V_{in} = V_{out} \left[\left(1 + \frac{Z_2}{Z_4} \right) + \frac{Z_1 Z_2}{Z_3 Z_4} + \frac{Z_1}{Z_4} \right]$$

$$= V_{out} \left(\frac{Z_3 Z_4 + Z_2 Z_3 + Z_1 Z_3 + Z_1 Z_4}{Z_3 Z_4} \right)$$

Show examples.

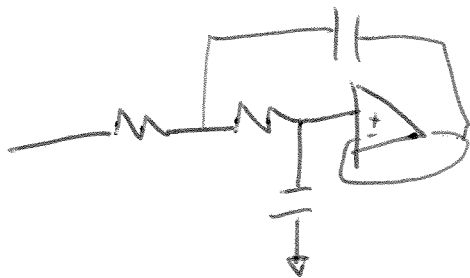

and

